

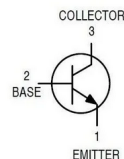


2


2N2222

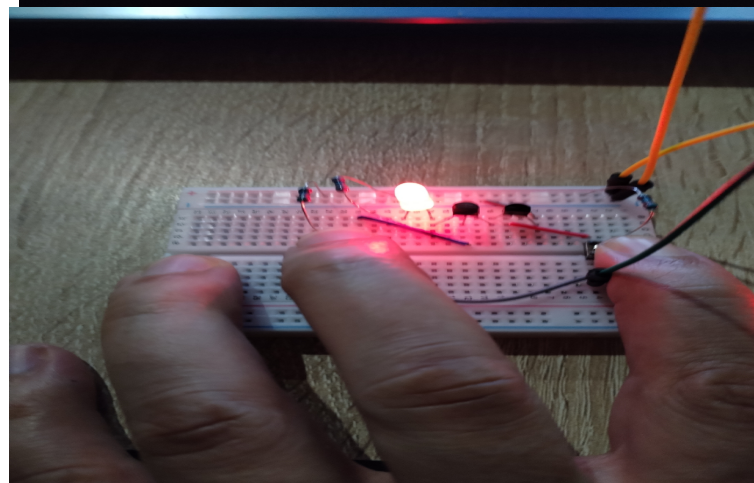

PORTA AND		
Input		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

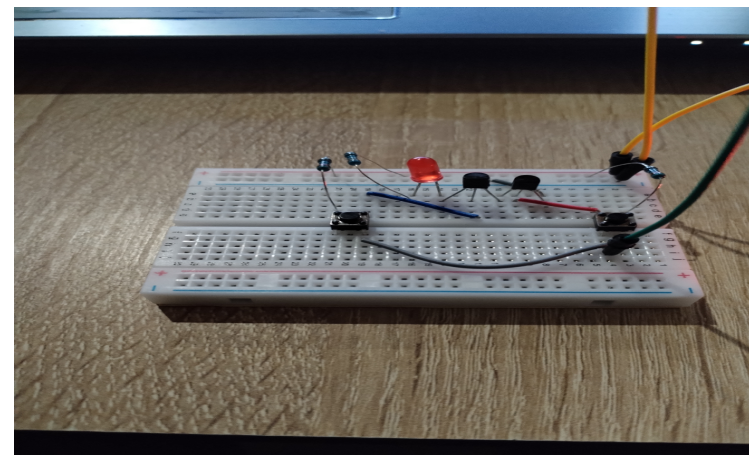

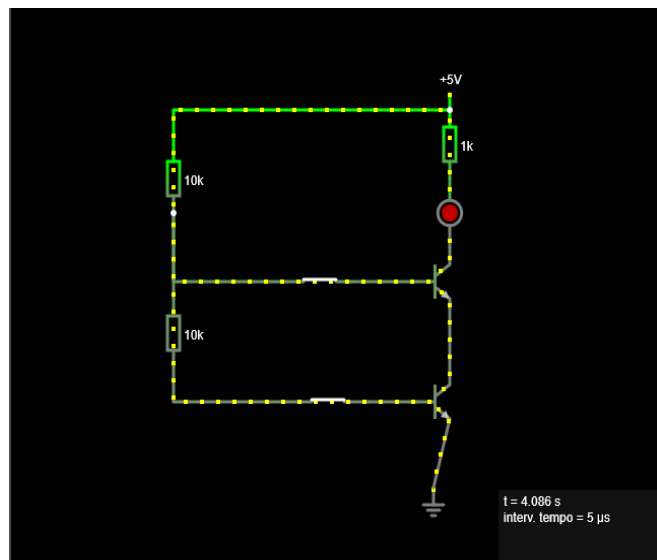Na lógica o LED irá acender com os dois botões pressionados



Schematic	Schematic1		Create at	2025-03-15
Board	Board1		Update at	2025-03-15
Drawn		New Project ufcd 6024 2(4)		
Reviewed				
		Version	Size	Page 1 Total 1
		V1.0	A4	EasyEDA.com